

Mid-Semester Examination

BitCounter using the Krypton CPLD

Dhruv Ilesh Shah — 150070016

March 18, 2017

Overview

In this experiment, we were expected to design a combinational circuit which calculates the number of input bits that are high, in a 16-bit input.

The code was compiled on Quartus Prime, and simulated using ModelSim. GHDL was also used for simulation purposes, at a low level. This was then uploaded to the *Krypton v1.1* 5M1270ZT144C5 CPLD-based board.

The algorithm and setup has been covered in section 1. We implement the counter in a parallel fashion, significantly reducing gate delays. The VHDL codes have been kept modular and as generic as possible, for reusability and code clarity. Section 2 presents the simulation observations and miscellaneous results. Section 3 presents the observations after running the scan-chain test on the board.

1 Setup & Algorithm

The task is pretty trivial, and using a serial adder to add the 16 bits, although straight-forward, can cause a large amount of delay in the computation. It is also inefficient, as are adding the bits *one at a time*. Instead, I used the following version of *Divide & Conquer*, specific to this case.

- Group the bits into four groups, of four bits each.
 - b15 ... b12 → int0
 - b11 ... b8 → int0
 - b7 ... b4 → int0
 - b3 ... b0 → int0
- Add the four bits in each group *individually* using the entity `four_bit_linear` which generates a 4-bit output. This takes time equivalent to 4 serial additions instead of 16. The factor of 4 is compensated in memory.
- Take these 4 groups of 4-bit sums, and pool them together using a `FourBitAdder` which is basically a full adder.

The advantage of the above algorithm is that it causes significantly lower gate delays, as 4 computations are now occurring in a parallel setup.

2 Observations

Here, I present the results of running RTL & Gate-Level Simulation on the design.

2.1 RTL Simulation

```
# ** Note: SUCCESS, all tests passed.  
#   Time: 6815744 ns   Iteration: 0   Instance: /testbench
```

Figure 1: RTL Simulation Result for the BitCounter

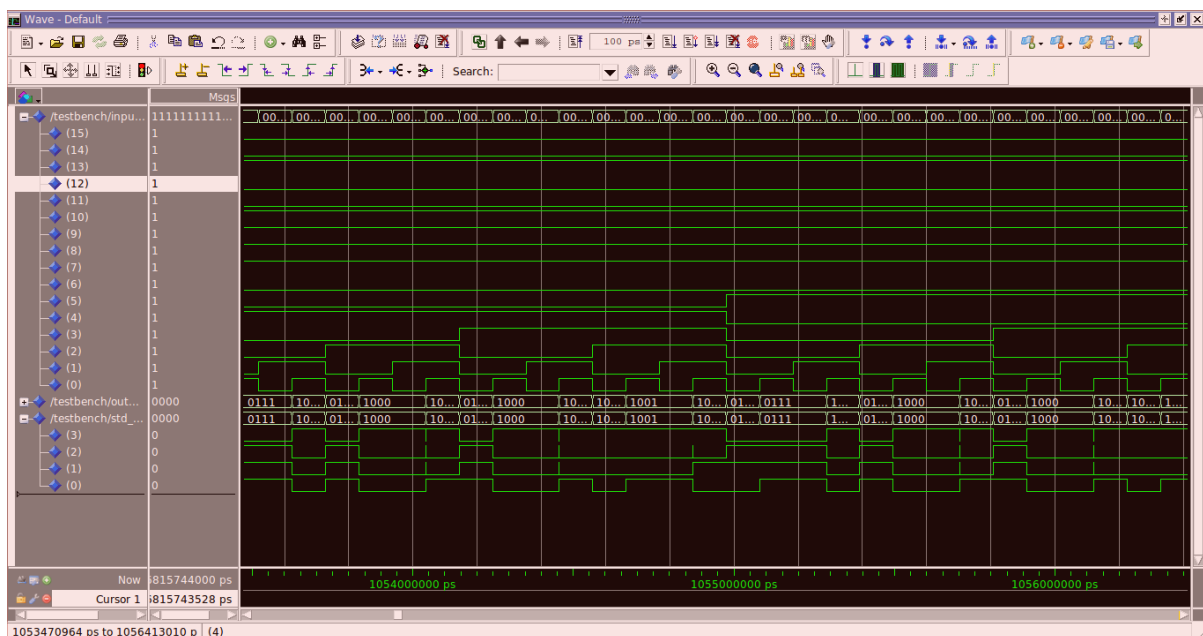


Figure 2: A snapshot RTL Simulation waveform on the BitCounter

2.2 Gate-Level Simulation

```
# ** Note: SUCCESS, all tests passed.  
#   Time: 6815744 ns   Iteration: 0   Instance: /testbench
```

Figure 3: Gate-Level Simulation Result for the BitCounter

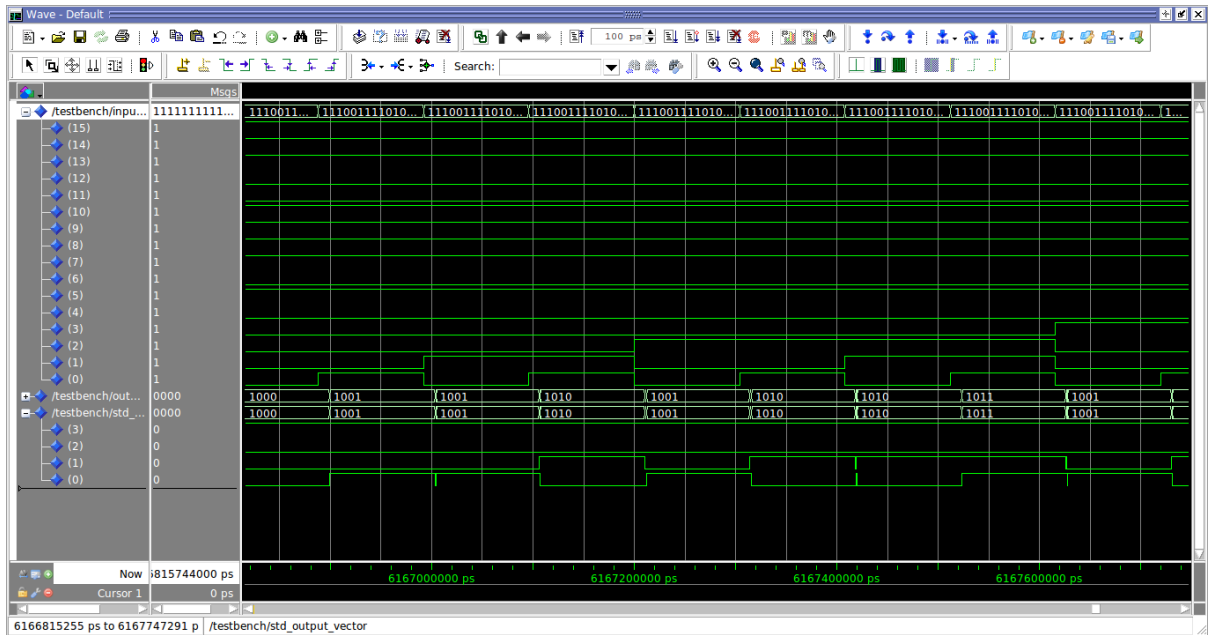


Figure 4: A snapshot gate-Level Simulation waveform on the BitCounter

3 Scan-Chain Tests

```
#----- Command - 131071 : SDR 16 TDI(FFFF) 4 TD0(0) MASK(F) -----#
Successfully entered the input..
Sampling out data..
----Success for F
Output Comparison : Success

#----- Command - 131072 : RUNTEST 1 MSEC -----#
Sampling out data..
----Success for 0
Output Comparison : Success
OK. All Test Cases Passed.
Transaction Complete.
```

Figure 5: Result of running an exhaustive Scan Chain test on the board.

For the sake of completeness, Figure 6 shows output screens after running the Gate-Level (left) and Scan-Chain (right) tests.

OUTPUTS.txt	out.txt
0000000010010100 0011	4 4 Success
0000000010010101 0100	5 5 Success
0000000010010110 0100	5 5 Success
0000000010010111 0101	6 6 Success
0000000010011000 0011	5 5 Success
0000000010011001 0100	6 6 Success
0000000010011010 0100	6 6 Success
0000000010011011 0101	7 7 Success
0000000010011100 0100	3 3 Success
0000000010011101 0101	4 4 Success
0000000010011110 0101	4 4 Success
0000000010011111 0110	5 5 Success
0000000010100000 0010	4 4 Success
0000000010100001 0011	5 5 Success
0000000010100010 0011	5 5 Success
0000000010100011 0100	6 6 Success
0000000010100100 0011	4 4 Success
0000000010100101 0100	5 5 Success
0000000010100110 0100	5 5 Success
0000000010100111 0101	6 6 Success
0000000010101000 0011	5 5 Success
0000000010101001 0100	6 6 Success
0000000010101010 0100	6 6 Success
0000000010101011 0101	7 7 Success
0000000010101100 0100	4 4 Success
0000000010101101 0101	5 5 Success
0000000010101110 0101	5 5 Success
0000000010101111 0110	6 6 Success
0000000010110000 0011	5 5 Success
0000000010110001 0100	6 6 Success

Figure 6: Output screens after running the Gate-Level (left) and Scan-Chain (right) test.

Conclusion

Starting from the very scratch, in this report, I have presented the logic and code for a combinational implementation of a bit counter. The logic was tested using RTL simulation, followed by the gate-level simulation for delay analysis and emulating the CPLD. This was followed by an actual rigorous test on the CPLD board after burning the code on it, using the *TIVA-C* microcontroller.

All the cases passed successfully at all stages and hence the complete bit counter can be used in hardware, as required.